



EE4105: Project Report

A report submitted to the
Department of Electrical and Information Engineering
Faculty of Engineering
University of Ruhuna
Sri Lanka

On 29th of April 2024

In completing the report for the module
EE4105 Electronic Project

By: Group G36

| | |
|----------------------|----------------|
| Kodikara A.W | - EG/2021/4613 |
| Kodithuwakku K.K.A.M | - EG/2021/4614 |
| Koshala M.P.S. | - EG/2021/4617 |
| Kularathna H.E. | - EG/2021/4619 |

Contents

| | | |
|-----|---------------------------------|----|
| 1 | Introduction | 4 |
| 1.1 | Problem Statement | 4 |
| 1.2 | Objectives | 4 |
| 1.3 | Methodology | 5 |
| 2 | Design of the amplifier | 6 |
| 2.1 | Required components | 6 |
| 2.2 | Mathematical calculations | 7 |
| 3 | Implementation of the circuit | 10 |
| 3.1 | Captures of Schematic | 10 |
| 3.2 | PCB Layout Design | 10 |
| 3.3 | 3D View of the Circuit | 11 |
| 3.4 | Practically implemented circuit | 11 |
| 4 | Results | 13 |
| 4.1 | Proteus simulation results | 13 |
| 5 | Discussion | 14 |

List of Figures

| | |
|---|----|
| Figure 2-1 : Datasheet of BC547BP Transistor | 6 |
| Figure 2-2 : Calculating beta value using proteus schematic | 8 |
| Figure 2-3 : Observations for calculate β Value | 8 |
| Figure 3-1 : 3D View of the Amplifier | 11 |

1 Introduction

Amplifiers, such as the common emitter BJT amplifiers, are essential components in electronics, increasing the strength of input signals to produce larger output signals with the same waveform. Proper biasing of transistors is crucial for amplifier functionality, ensuring correct operation and signal integrity. With applications ranging from broadcasting to wireless technology and audio equipment, amplifiers play a fundamental role in signal processing and transmission.

1.1 Problem Statement

Here we have to implement a Common Emitter BJT Amplifier with the following specifications.

- Voltage gain = 270
- Bandwidth = 6.5 MHz

1.2 Objectives

1. Analyze the structure and operational principles of BJT amplifiers.
2. Determine component values, including resistors and capacitors, to meet specified requirements (Gain and Bandwidth).
3. Create a schematic and simulate the common emitter amplifier circuit design in Proteus.
4. Employ PCB layout using Proteus to implement the amplifier circuit and visualize it in 3D.
5. Analyze and contrast theoretical values with experimental outcomes.

1.3 Methodology

1. Researching BJT common emitter amplifier to derive component values according to specifications.
2. Choosing suitable component according to derived values and assumptions.
3. Calculating to determine component values based on specified characteristics.
4. Simulating the design using Proteus software.
5. Addressing any issues and refining the design.
6. Implementing the circuit design on a printed circuit board using Proteus software.
7. Evaluating both theoretical and practical performance of the design and summarizing important points in the report conclusion.

2 Design of the amplifier

2.1 Required components

| ABSOLUTE MAXIMUM RATINGS | | | | | | |
|--------------------------|---|------------|------------------|--|--|--|
| Symbol | Parameter | Value | Unit | | | |
| V_{CBO} | Collector-Base Voltage ($I_E = 0$) | 50 | V | | | |
| V_{CEO} | Collector-Emitter Voltage ($I_B = 0$) | 45 | V | | | |
| V_{EBO} | Emitter-Base Voltage ($I_C = 0$) | 6 | V | | | |
| I_C | Collector Current | 100 | mA | | | |
| I_{CM} | Collector Peak Current | 200 | mA | | | |
| P_{tot} | Total Dissipation at $T_C = 25^\circ\text{C}$ | 500 | mW | | | |
| T_{stg} | Storage Temperature | -65 to 150 | $^\circ\text{C}$ | | | |
| T_J | Max. Operating Junction Temperature | 150 | $^\circ\text{C}$ | | | |

| | | | | | | |
|-----------------|---------------------------------|---|--|------------|------------|-------------|
| $V_{BE(sat)}^*$ | Base-Emitter Saturation Voltage | $I_C = 10\text{ mA}$ $I_C = 100\text{ mA}$ | $I_B = 0.5\text{ mA}$ $I_B = 5\text{ mA}$ | | 0.7 0.9 | |
| $V_{BE(on)}^*$ | Base-Emitter On Voltage | $I_C = 2\text{ mA}$ $I_C = 10\text{ mA}$ | $V_{CE} = 5\text{ V}$ $V_{CE} = 5\text{ V}$ | 0.58 | 0.66 | 0.7 0.77 |
| h_{FE} | DC Current Gain | $I_C = 2\text{ mA}$ for BC547B for BC547C | $V_{CE} = 5\text{ V}$ | 200 420 | | 450 800 |
| f_T | Transition Frequency | $I_C = 10\text{ mA}$ | $V_{CE} = 5\text{ V}$ $f = 100\text{ MHz}$ | 100 | | |

Figure 2-1 : Datasheet of BC547BP Transistor

As seen in the above [Figure 2-1](#) data sheet the BC547BP transistor is well selected for our amplifier circuit in order to obtain the given specifications (Gain 270, Bandwidth 6.5MHz). Therefore we used BC547BP transistor for our circuit.

From calculations we obtain the resistor and capacitors values according to the given specifications. Therefore, the standard resistors and capacitors we used for the circuit are as follows,

Resistors,

- $R_C = 1800\Omega$
- $R_E = 1k\Omega$
- $R_1 = 15k\Omega$
- $R_2 = 5.6k\Omega$
- $R_3 = 15\Omega$

Capacitors,

- $C_1 = 1\mu\text{F}$
- $C_2 = 1\mu\text{F}$
- $C_E = 220\mu\text{F}$
- $C_3 = 1n\text{F}$

2.2 Mathematical calculations

According to the transistor output characteristics let's take $V_{CE} = 8V$,

$$\frac{V_{CC}}{2} \geq V_{CE}$$

$$\frac{V_{CC}}{2} \geq 8V$$

$$V_{CC} \geq 12V$$

Then let's select $V_{CC} = 20V$

Also let's take $I_C = 4mA$,

$$r_e = \frac{26 mV}{I_C}$$

$$r_e = \frac{26 mV}{4 mA}$$

$$r_e = 6.5 \Omega$$

$$\text{Gain} = \frac{R_C}{r_e}$$

$$270 = \frac{R_C}{6.5 \Omega}$$

$$R_C = 1755 \Omega$$

Using Kirchhoff's voltage law,

$$V_{CC} = I_C R_C + I_E R_E + V_{CE}$$

When $V_{CE} = 0$,

$$20V = 4 \times 10^{-3} \times 1755 + 4 \times 10^{-3} \times R_E$$

(Assume that $I_C = I_E$ as I_B is really small)

$$R_E = 1245 \Omega$$

$$\begin{aligned} V_E &= I_E R_E \\ &= 4 \times 10^{-3} A \times 1245 \Omega \\ &= 4.98 V \end{aligned}$$

$$\begin{aligned} V_B &= 0.7V + V_E \\ &\text{(Bias voltage 0.7V for Si transistor)} \end{aligned}$$

$$V_B = 0.7V + 4.98V$$

$$V_B = 5.68V$$

Since I_B is small,

$$\frac{R_1}{R_1 + R_2} \times V_{CC} = V_B$$

$$\frac{R_1}{R_1 + R_2} \times 20V = 5.68$$

$$5.68R_1 = 14.32R_2$$

Let's take $R_1 = 14.32k\Omega$ and $R_2 = 5.68k\Omega$

Let's calculate β value,

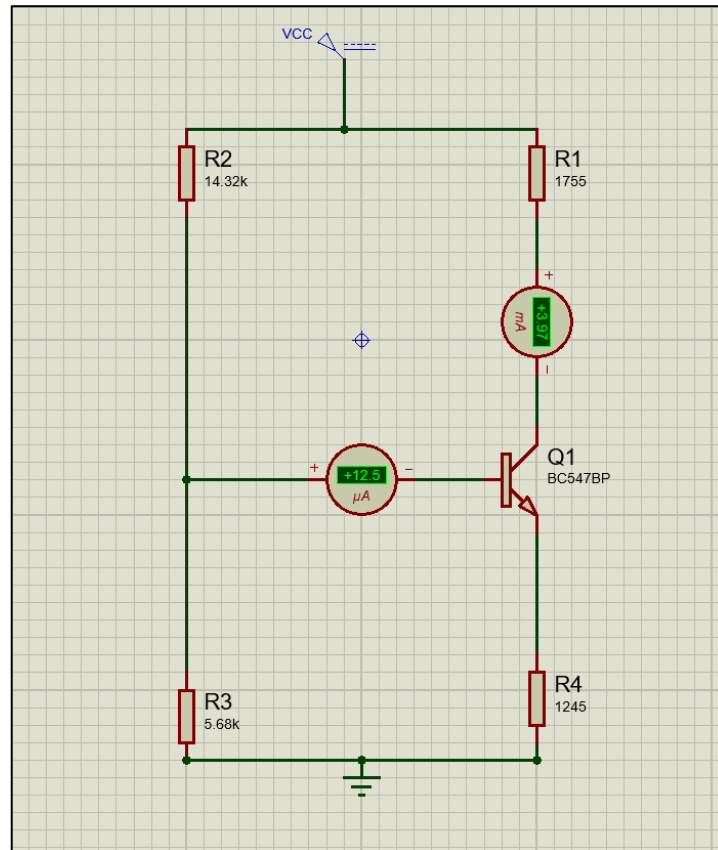


Figure 2-2 : Calculating beta value using proteus schematic

Using the above I_C and I_B values we can calculate the β value,

$$\beta = \frac{I_C}{I_E}$$

$$\beta = \frac{3.97 \times 10^{-3}}{12.5 \times 10^{-6}}$$

$$\beta = 317.6$$

$$R_{eq1} = R_1 // R_2 // \beta r_e$$

$$R_{eq1} = 1.37 k\Omega$$

Assume $F_L = 100\text{Hz}$ and $F_H = 6.5001\text{MHz}$

$$C_1 = \frac{1}{2\pi f R_{eq1}}$$

$$C_1 = \frac{1}{2\pi \times 100 \times 1.37 \times 10^3}$$

$$C_1 = 1.16 \mu F$$

$$R_{eq2} = R_E // r_e$$

$$R_{eq2} = 6.466 \Omega$$

$$C_E = \frac{1}{2\pi f R_c}$$

$$C_E = \frac{1}{2\pi \times 100 \times 6.466}$$

$$C_E = 246.14 \mu F$$

$$R_{eq3} = R_c = 1755 \Omega$$

$$C_2 = \frac{1}{2\pi f R_c}$$

$$C_2 = \frac{1}{2\pi \times 100 \times 1755}$$

$$C_2 = 0.907 \mu F$$

Let's calculate the low pass filter values,

$$C_{LPF} = 1nF$$

$$R_{LPF} = \frac{1}{2\pi f C_{LPF}}$$

$$R_{LPF} = \frac{1}{2\pi \times 6.5 \times 10^6 \times 1 \times 10^{-9}}$$

$$R_{LPF} = 24.485 \Omega$$

3 Implementation of the circuit

3.1 Captures of Schematic

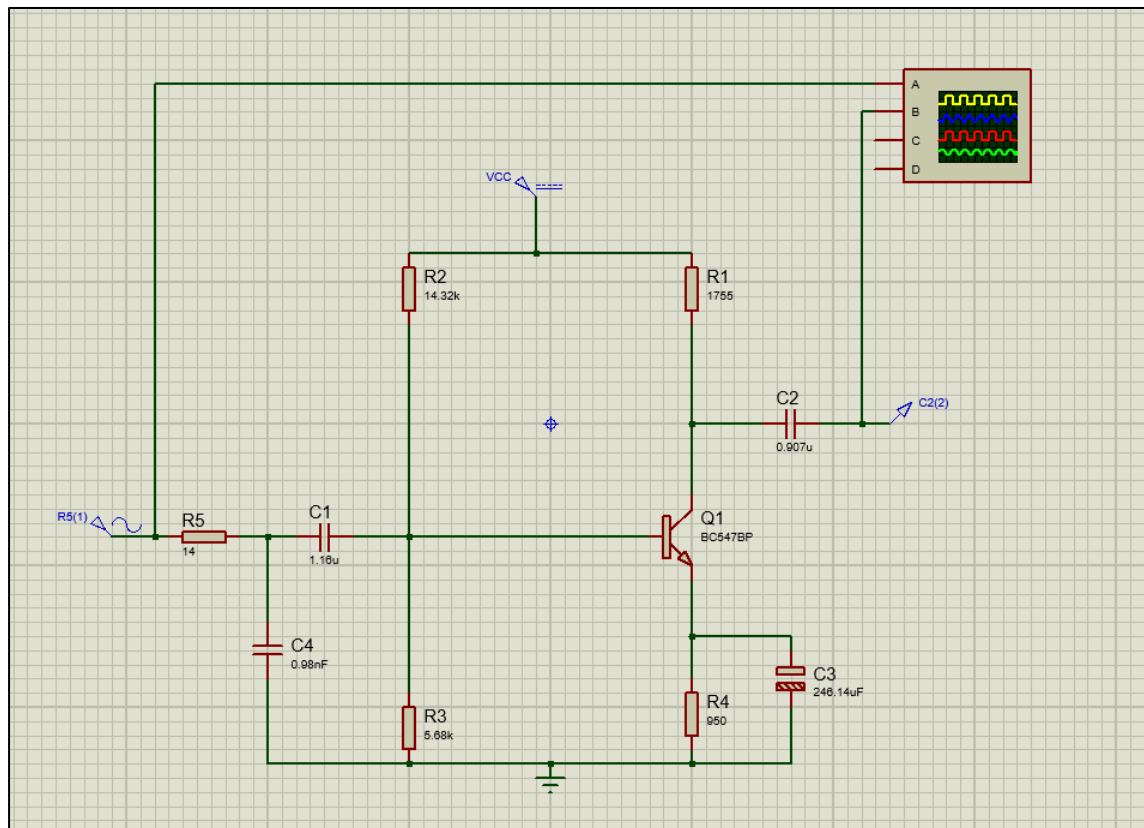


Figure 3-1 : Proteus schematic design of BJT amplifier

3.2 PCB Layout Design

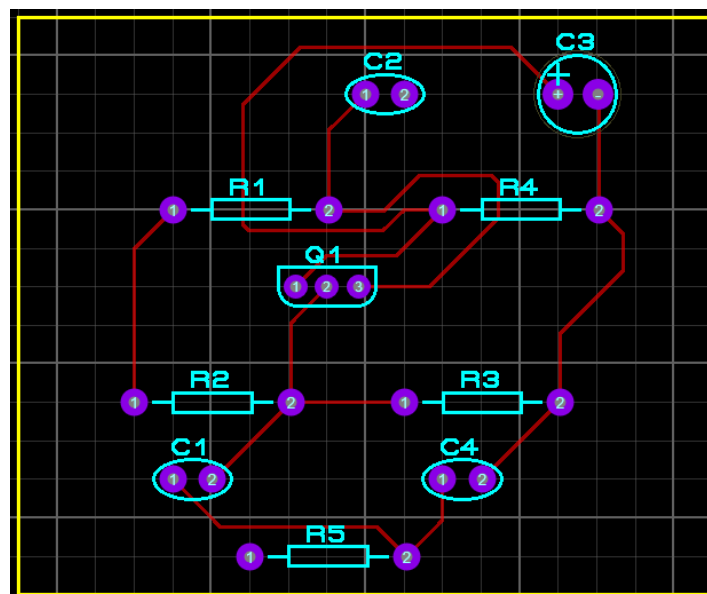


Figure 3-2 : PCB layout of design

3.3 3D View of the Circuit

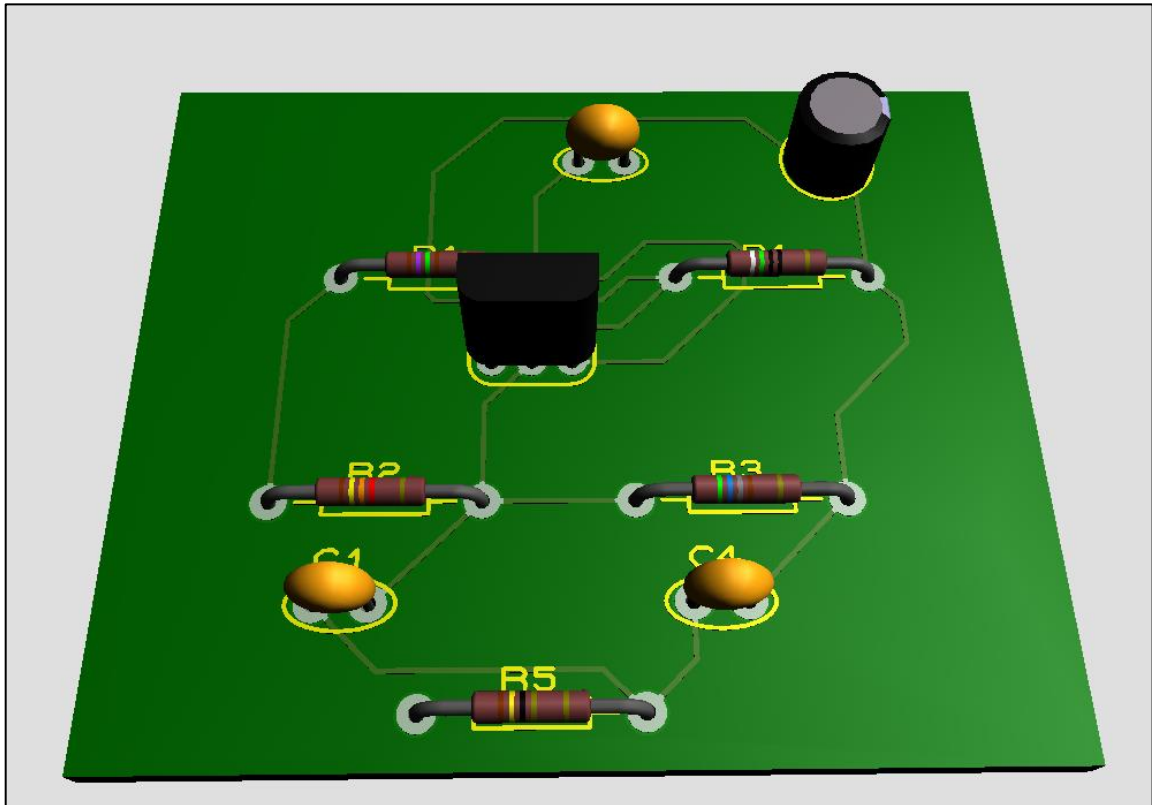


Figure 3-3 : 3D view of design amplifier

3.4 Practically implemented circuit

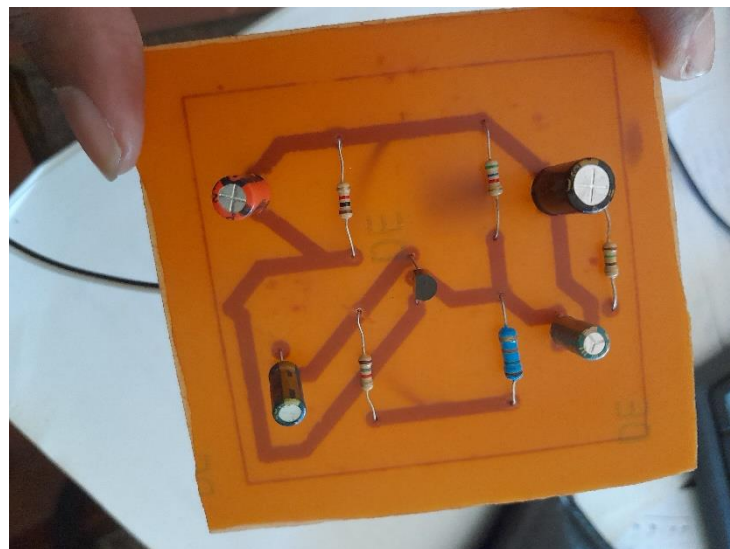


Figure 3-4 : Top View of the Implemented PCB

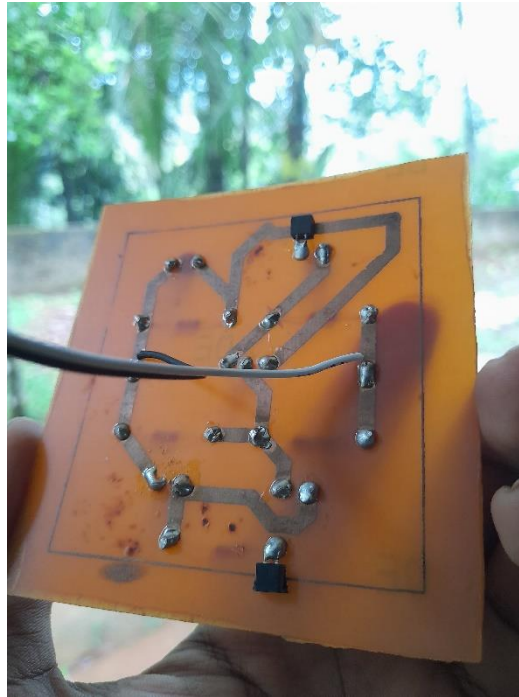


Figure 3-5 : Bottom View of the Implemented PCB

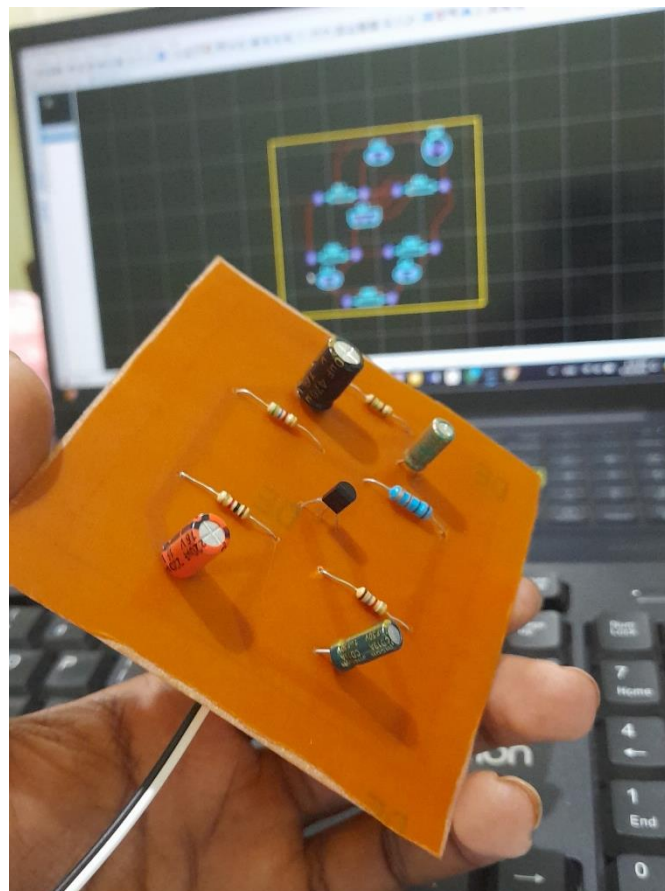


Figure 3-6 : PCB with all components

4 Results

4.1 Proteus simulation results

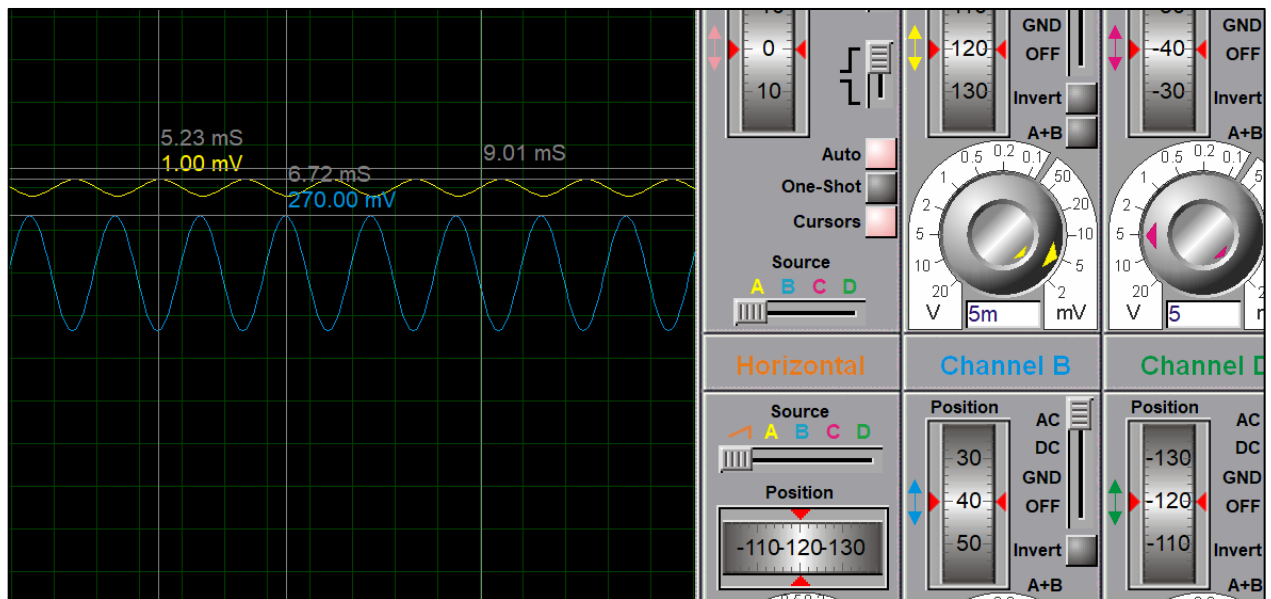


Figure 4-1 : Oscilloscope Output in Proteus

$$V_{IN} = 1mV$$

$$V_{out} = 270mV$$

$$Gain = \frac{V_{out}}{V_{IN}}$$

$$Gain = \frac{270mV}{1mV} = 270$$

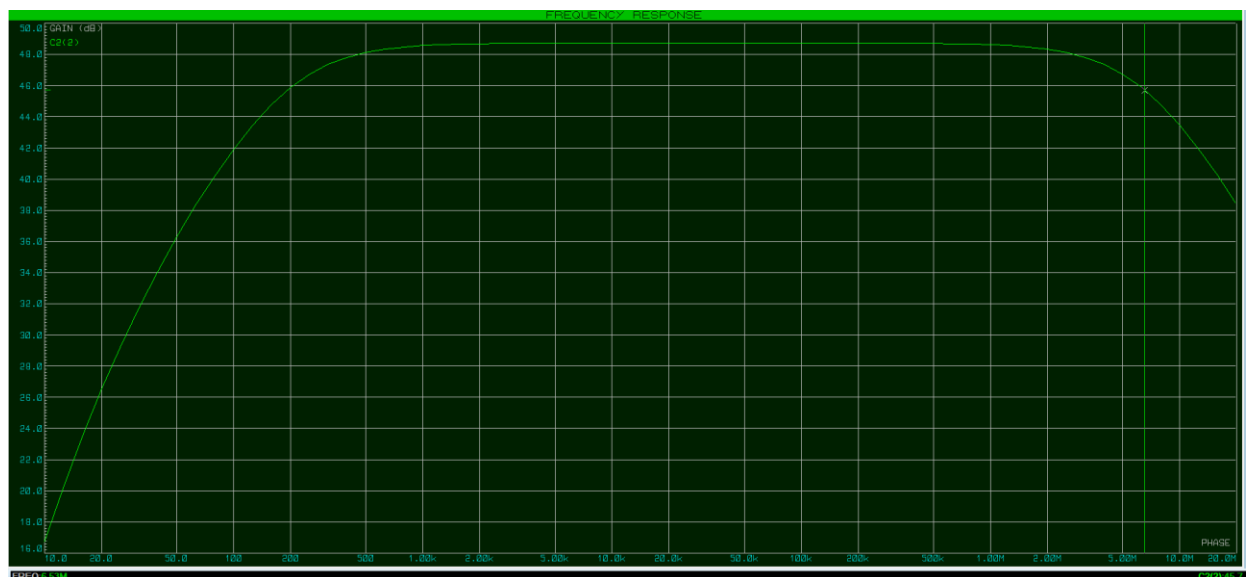


Figure 4-2 : Frequency Response for the Final Circuit

Pass Band Gain = 48.7

Low Cutoff Frequency = 45.7 at 192Hz

High Cutoff Frequency = 45.7 at 6.53MHz

Bandwidth of the Amplifier = 6.53MHz – 192Hz

Bandwidth of the Amplifier = 6.53MHz

5 Discussion

In the theoretical values it gives the gain as 48.63dB value, but in the proteus simulation it gives the gain as 48.7dB. And also, the bandwidth of the amplifier also we couldn't be able to obtain the exact value. Main reason might be the deviation of the values could be the calculated resistors and capacitors values are not compatible with the standard resistors and capacitors values. And also, we did the testing under the normal conditions, but the transistors are properly working on the special conditions as given in the data sheet. Those may be some of the result for the deviation of the gain and bandwidth values.

When we compare the theoretical values with experimental values , we can notice that there is a considerable difference with expected and observed values as we had to use approximated valued capacitors and resistors for our PCB.